

Chapter 1 - Basics

- **Electric current = (i):** time rate of change of charge, measured in amperes (A).
- **Charge = (q):** integral of i
- **Voltage (or potential difference) = (V):** energy required to move a unit charge through an element
- **Power = (W):** $v_i = (i^2)R$
- **Passive sign convention:** when the current enters through the positive terminal of an element ($p = +v_i$)

Remember:
+Power absorbed = -Power supplied --> sum of power in a circuit = 0

- **Energy (J)** = integral of P

Chapter 2

Ohms Law: $v=iR$
Conductance (G) = $1/R = i/v$
Branch: single element such as a voltage source or a resistor.
Node: point of connection between two or more branches
Loop: any closed path in a circuit.
Kirchhoff's current law (KCL): algebraic sum of currents entering a node (or a closed boundary) is zero.

Chapter 2 (cont)

Kirchhoff's voltage law (KVL): algebraic sum of all voltages around a closed path (or loop) is zero.

Voltage D: $v_1 = ((R_1) / (R_1 + R_2)) * v$
Voltage D: $v_2 = ((R_2 / (R_1 + R_2)) * v$
Current D: $i_1 = (R_2 * i) / (R_1 + R_2)$
Current D: $i_2 = (R_1 * i) / (R_1 + R_2)$

Chapter 3 - Methods of Analysis

Nodal Analysis: want to find the node voltages
 Step 1: select reference node
 - assign voltages $v_1 \rightarrow v_n$ to remaining nodes
 Step 2: apply KCL to each node
 - want to express branch currents in terms of voltage
 Step 3: solve for unknowns
Important:
current flows from high to low (+ ==> -)
SuperNode Properties
 1. The voltage source inside the supernode provides a constraint equation needed to solve for the node voltages
 2. Supernode had no voltage of its own
 3. Supernode requires the application of both KCL and KVL
Mesh Analysis

Chapter 3 - Methods of Analysis (cont)

Step 1:
Assign mesh currents or loops
 Step 2:
Apply KVL
 - use OHMS LAW to express voltages in terms of the mesh current
 Step 3:
Solve for the unknown
Supermesh
 - when two meshes have an independent or dependent CURRENT source between them

Chapter 4 - Circuit Theorems

Superposition
 principal states that the VOLTAGE ACROSS or CURRENT THROUGH an element in a linear circuit is the SUM of the VOLTAGES OR CURRENTS that are caused after solving for each INDEPENDENT source separately
How to solve a superposition circuit
 Step 1: Turn OFF ALL independent sources except for ONE ==> find voltage or current
 Step 2: Repeat above for all other independent sources
 Step 3: Add all voltages/currents together to find final value
Thevenin's Theorem
 $V(th) = V(oc)$

Chapter 4 - Circuit Theorems (cont)

circuit with Load: $I(L) = V(th) / (R(th) + R(L)) \Rightarrow V(L) = R(L) / (L) \Rightarrow (R(L) / ((R(th) + R(L)) V(th))$
Norton's Theorem
 $R(n) = R(th)$
 $I(n) = i(sc) \Rightarrow (sc) = \text{short circuit}$
 $I(n) = V(th) / R(th)$
Maximum Power Transfer
 max power is transferred to the LOAD RESISTOR when the LOAD RESISTOR is EQUAL to the THEVENIN RESISTANCE:
 $R(L) = R(th)$
 $p(max) = V(th)^2 / 4R(th)$

Chapter 6 - Capacitors and Inductors

Capacitors
 $q = C * v$
capacitance: ratio of the charge on one plate to the voltage difference between the two plates
 $i(t) = C(dv/dt)$
 $v(t) = 1/C [\text{Integral: } i(T)dT + v(t_0)]$
 T = time constant
 energy (w) = $.5Cv^2$
Important:
VOLTAGE of a capacitor cannot change instantaneously
Capacitors in Series: $1 / Ceq = 1/C_1 + 1/C_2 + 1/C_n$
Capacitors in Parallel: $Ceq = C_1 + C_2 + C_n$
Inductors
 $v = L(di / dt)$

Chapter 6 - Capacitors and Inductors (cont)

$i = (1/L) \int (v(t)dt + i(t_0))$
energy (w) = $.5Li^2$

Important:

CURRENT through an inductor cannot change instantaneously

Inductors in Series:

$Leq = L1 + L2 + Ln$

Inductors in Parallel:

$1/Leq = 1/L1 + 1/L2 + 1/Ln$

Chapter 7 - First Order Circuits

Source Free RC Circuits

$v(t) = V0 * e^{-t/T} \Rightarrow T = RC$

How to Solve SOURCE FREE RC CIRCUITS

Step 1: Find $v0 = V0$ across the capacitor

Step 2: Find T (time constant)

Source Free RL Circuits

$i(t) = I0 * e^{-t/T} \Rightarrow T = L / R$

$vr(t) = iR = I0 * Re^{-t/T}$

How to Solve SOURCE FREE RL CIRCUITS

Step 1: Find $i(0) = I0$ through the inductor

Step 2: Find T (time constant)

Step response of an RC circuit

$v(t) = V0$ when $t < 0$

$v(t) = Vs + (V0 - Vs)e^{-t/T}$ when $t > 0$

$v = vn + vf \Rightarrow vn = V0e^{-t/T}, vf = Vs(1 - e^{-t/T})$

OR

$v(t) = v(\text{infinity}) + [(v(0) - v(\text{infinity}))e^{-t/T}]$

Chapter 7 - First Order Circuits (cont)

How to solve a STEP

RESPONSE OF AN RC CIRCUIT

Step 1: Find initial capacitor voltage $v0$ ($t < 0$)

Step 2: Find final capacitor voltage $v(in)$ ($t > 0$)

Step 3: Find T (time constant) ($t > 0$)

Step response of an RL circuit

$i(t) = i(\text{infinity}) + [i(0) - i(\text{infinity})]e^{-t/T}$

How to solve a STEP

RESPONSE OF AN RL CIRCUIT

Step 1: Find initial inductor current $i0$ ($t = 0$)

Step 2: Find final inductor current $i(inf) \Rightarrow (t > 0)$

Step 3: Find T (time constant) ($t > 0$)

Chapter 8 - Second Order Circuits

Source Free RLC Circuits

$v(0) = 1/C \int (idt = v0)$ from 0 to -infinity]

$i(0) = I(0)$

Determining Dampness

$(\alpha) = R / (2L)$

$(\omega w0) = 1 / \sqrt{LC}$

1 - Overdamped ($\alpha > w0$)

$i(t) = Ae^{s1t} + Be^{s2t}$

2 - Critically Damped ($\alpha = w0$)

$s1 = s2 = a$

$i(t) = (A + Bt)e^{-at}$

3 - Underdamped ($\alpha < w0$)

$i(t) = e^{-at}(A \cos(w0t) + B \sin(w0t))$

Chapter 8 - Second Order Circuits (cont)

Source Free Parallel Circuits

roots of characteristic equation

$s1,2 = -a \pm \sqrt{a^2 + w0^2}$

$a = 1/(2RC)$

$w0 = 1/\sqrt{LC}$

1 - Overdamped ($\alpha > w0$)

$i(t) = Ae^{s1t} + Be^{s2t}$

2 - Critically Damped ($\alpha = w0$)

$s1 = s2 = a$

$i(t) = (A + Bt)e^{-at}$

3 - Underdamped ($\alpha < w0$)

$i(t) = e^{-at}(A \cos(wd(t)) + B \sin(wd(t)))$

Step Response of a SERIES RLC Circuit

1 - Overdamped ($\alpha > w0$)

$v(t) = Vs + Ae^{s1t} + Be^{s2t}$

2 - Critically Damped ($\alpha = w0$)

$s1 = s2 = a$

$v(t) = Vs + (A + Bt)e^{-at}$

3 - Underdamped ($\alpha < w0$)

$v(t) = Vs + e^{-at}(A \cos(wd(t)) + B \sin(wd(t)))$

Step Response of a PARALLEL RLC Circuit

1 - Overdamped ($\alpha > w0$)

$i(t) = Is + Ae^{s1t} + Be^{s2t}$

2 - Critically Damped ($\alpha = w0$)

$s1 = s2 = a$

$i(t) = Is + (A + Bt)e^{-at}$

3 - Underdamped ($\alpha < w0$)

$i(t) = Is + e^{-at}(A \cos(wd(t)) + B \sin(wd(t)))$

Chapter 9 - Sinusoids and Phasors

$w = \omega$

$T = 2\pi / w$

freq = $1 / T$ (Hertz)

$v(t) = v(m) \sin(wt + \theta)$

$v1(t) = v(m) \sin(wt)$

$v2(t) = v(m) \sin(wt + \theta)$

$\sin(A \pm B) = \sin A \cos B \pm$

$\cos A \sin B$

$\cos(A \pm B) = \cos A \cos B \pm$

$\sin A \sin B$

$A \cos(wt) + B \sin(wt) = C \cos(wt - \theta)$

$C = \sqrt{A^2 + B^2}$

$\theta = \tan^{-1}(B/A)$

Complex Numbers

rectangular form: $z = x + jy$

polar: $z = r \angle (\theta)$

expolar: $z = re^{j(\theta)}$

$\sin: r(\cos(\theta) + j \sin(\theta))$

$z = x + jy$

$z1 = x1 + jy1 \Rightarrow r1 \angle (\theta1)$

$z2 = x2 + jy2 \Rightarrow r2 \angle (\theta2)$

operations

addition: $z1 + z2 \Rightarrow (x1 + x2) +$

$j(y1 + y2)$

subtraction: $z1 - z2 \Rightarrow (x1 - x2) +$

$j(y1 - y2)$

multiplication: $z1z2 \Rightarrow r1r2 \angle$

$((\theta1) + (\theta2))$

division: $z1/z2 \Rightarrow r1/r2 \angle$

$((\theta1) - (\theta2))$

reciprocal: $1/z = 1/r \angle -(\theta)$

square: $\sqrt{z} = \sqrt{r} \angle$

$(\theta)/2$

Chapter 9 - Sinusoids and Phasors (cont)

complex conjugate: $z^* = x - jy = r < -(\theta)$
 $= re^{-j(\theta)}$

real vs. imaginary

$e^{+j(\theta)} = \cos(\theta) + j\sin(\theta)$
 $e^{-j(\theta)} = \cos(\theta) - j\sin(\theta)$

$\cos(\theta) = \text{REAL}$

$j\sin(\theta) = \text{IMAGINARY}$

voltage-current relationship

$R v = R i$ (time domain) $v = R i$

(frequency domain)

$L v = L(di/dt)$ (time) $v = j\omega L i$

$C i = C(dv/dt)$ (time) $V = I / j\omega C$

Impedance vs. admittance

$R Z = R$ (impedance) $Y = 1 / R$

$L Z = j\omega L$ $Y = 1 / j\omega L$

$C Z = 1 / j\omega C$ $Y = j\omega C$

Complex Numbers with

Impedance

$Z = R + jX = |Z| < (\theta)$

$|Z| = \sqrt{R^2 + X^2}$

$(\theta) = \tan^{-1}(X / R)$

$R = |Z| \cos(\theta)$

$X = |Z| \sin(\theta)$

Chapter 10 - AC Circuits

Analyzing AC Circuits

Step 1: Transform circuit to phasor or frequency domain

Step 2: Solve Using Circuit

Techniques

Step 3: Transform phasor ==>

time domain



By Lini
cheatography.com/lini/

Published 8th May, 2015.
Last updated 12th May, 2016.
Page 3 of 3.

Sponsored by **Readable.com**
Measure your website readability!
<https://readable.com>