

Basic notations

current (I)	q/t
q	charge
V	terminal voltage
resistance (R)	V/I or $\rho l/A$

in the formula for resistance, the first formula has current and the second one has length of the resistor

Effect of stretching of wire on resistance

L -- original length of wire
 A -- original cross-sectional area
 L' -- length of wire after stretching
 A' -- cross-sectional area of wire after stretching
 final resistance, $R' = n^2R$

Resistors in Series

$V = IR(s)$ [R(s) is equivalent resistance for resistors in series]

general formula for 'n' resistors in series --

$$R(s) = R(1) + R(2) + R(3) + \dots + R(n)$$

$$\therefore R(s) = nR$$

n --- no. of equal resistors

Resistors in Parallel

$I = V/R(p)$ [R(p) is equivalent resistance for resistors in parallel]

general formula for 'n' resistors in parallel --

$$1/R(p) = 1/R(1) + 1/R(2) + 1/R(3) + \dots +$$

$$1/R(n)$$

$$\therefore R(p) = R/n$$

Kirchoff's Laws

1st Law :-

At any junction of several circuit elements, the sum of currents entering the junction must be equal to sum of currents leaving it.

2nd Law:-

The algebraic sum of changes in potential around any closed resistor loop must be zero.


Relation b/w R(s) & R(p)

$$R(s)/R(p) = n^2$$

Wheatstone Bridge

WHEATSTONE BRIDGE

BYJU'S
The Learning App

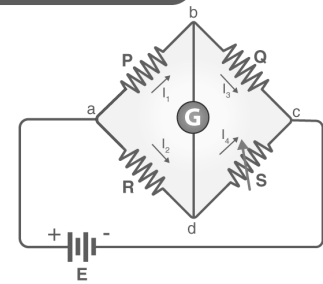

Here if,

$$P/R = Q/S \text{ or}$$

$$P/Q = R/S, \text{ then,}$$

we can simply remove G.

Now, P & Q are in series and R & S are in series, and the combination of the two are in parallel

C

By **Taneesha** (Taneesha)
cheatography.com/taneesha/

Published 5th November, 2023.
 Last updated 5th November, 2023.
 Page 1 of 1.

Sponsored by **Readable.com**
 Measure your website readability!
<https://readable.com>